

Quiz #3 : figure in Q#3 is not showing correctly
→ don't start if you have not yet
→ I will add the figure in the quiz pre-amble
→ I will add extra attempt (4)

CHAPTER 19:

19.1: ELECTRIC CURRENT

19.2: BATTERIES AND EMF

19.3: MAKING AND REPRESENTING SIMPLE CIRCUITS

19.4: OHM'S LAW

19.5: QUALITATIVE ANALYSIS OF CIRCUITS

19.6: JOULE'S LAW

19.7: KIRCHHOFF'S RULES

19.8 RESISTOR AND CAPACITOR CIRCUITS.

19.9 SOLVING CIRCUIT PROBLEMS

19.10: PROPERTIES OF RESISTORS

REVIEW

Ohm's Law: $\Delta V = IR$

Resistance: $R = \frac{\rho L}{A}$

Capacitor: $C = \frac{Q}{\Delta V}$

Joule's Law: $P = \left| \frac{\Delta U_q}{\Delta t} \right| = I\Delta V$


Kirchhoff's Loop Law:

$$\sum_{loop} \Delta V_i = 0$$

Kirchhoff's Junction (Node) Law:

$$\sum_{node} I_i = 0$$

19.8 DC CIRCUITS – RESISTORS IN SERIES

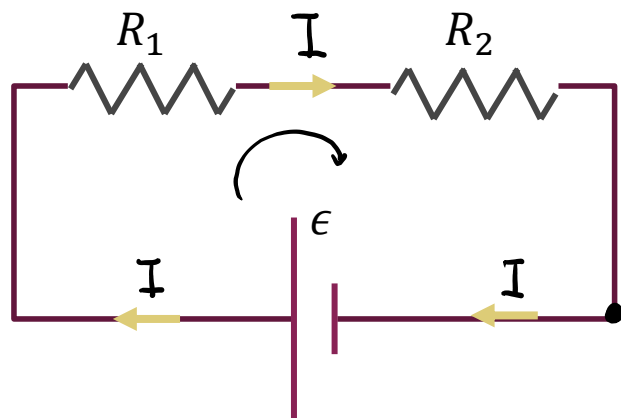

Current has only one way to go, so the current through each resistor is the same.

$$\epsilon - IR_1 - IR_2 = 0$$

$$\epsilon = \Delta V_1 + \Delta V_2$$


$$IR_{eq} = \underbrace{IR_1} + IR_2$$

$$R_{eq} = R_1 + R_2$$

IN SERIES

$$R_{eq} = \sum_{i=1}^N R_i$$

19.8 DC CIRCUITS – RESISTORS IN PARALLEL

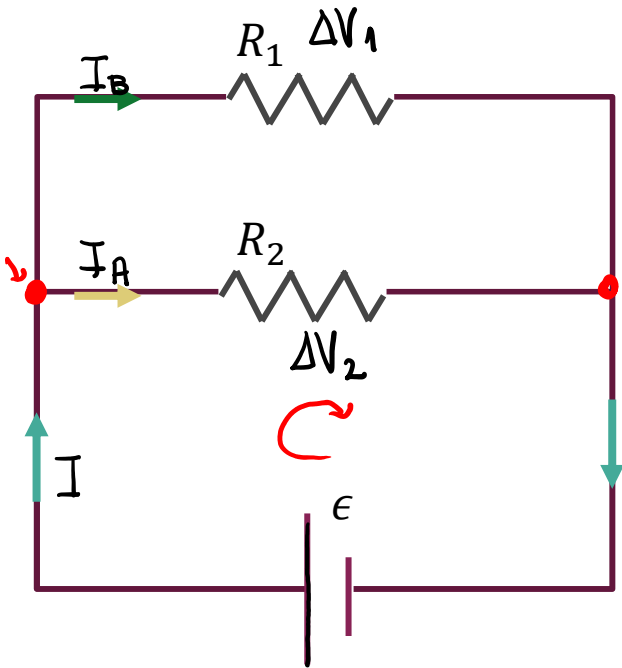

Current splits at the node, but potential difference across each resistor is the same:

$$-I_A R_2 + \epsilon = 0 \quad \text{1}$$

$$-I_B R_1 + \epsilon = 0$$

$$I_A + I_B = I$$

$$\Delta V_1 = \epsilon, \quad \Delta V_2 = \epsilon$$

$$I_A = \frac{\Delta V_2}{R_2} = \frac{\epsilon}{R_2}$$

$$I_B = \frac{\Delta V_1}{R_1} = \frac{\epsilon}{R_1}$$

$$R_{\text{TOTAL}} = R_{\text{equivalent}}$$

$$I = \frac{\epsilon}{R_{\text{TOT}}}$$


$$\frac{\epsilon}{R_{\text{eq}}} = \frac{\epsilon}{R_1} + \frac{\epsilon}{R_2} \rightarrow$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{\text{eq}}} = \sum_{i=1}^N \frac{1}{R_i}$$

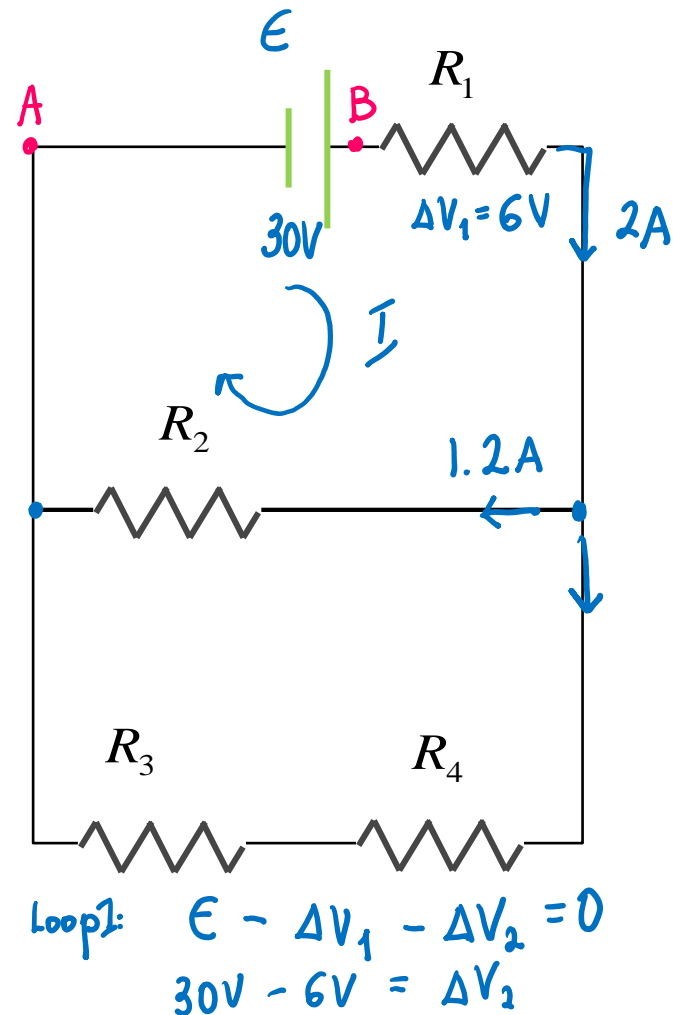EXAMPLE 19E – TRY

If the voltage of 30 V is applied between points A and B, what is the current through each resistor, voltage across each resistor and power dissipated by each one.



$R [\Omega]$	$V [V]$	$I [A]$	$P [W]$ $V \cdot I$
$R_1 = 3\Omega$	$\Delta V_1 = R_1 \cdot I_1$ 6V	2	12
$R_2 = 20\Omega$	$\Delta V_2 = 24V$	1.2	28.8
$R_3 = 18\Omega$	$0.8 \cdot 18$ 14.4	$2 - 1.2$ $= 0.8$	11.52
$R_4 = 12\Omega$	9.6	0.8	7.68
$R_{eq} = 15\Omega$	30V	$\frac{\epsilon}{R_{eq}} = 2$	60W




$$R_A = R_3 + R_4 = 18\Omega + 12\Omega = 30\Omega$$

R_2 & R_A in parallel

$$\frac{1}{R_B} = \frac{1}{R_2} + \frac{1}{R_A} = \frac{1}{20} + \frac{1}{30} = \frac{3}{60} + \frac{2}{60} = \frac{5}{60}$$


$$R_B = 12\Omega$$

$$R_{eq} = R_B + R_1 = 12\Omega + 3\Omega = 15\Omega$$

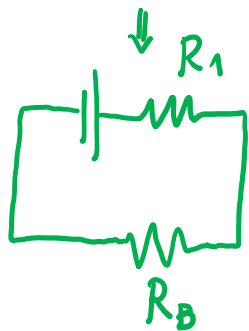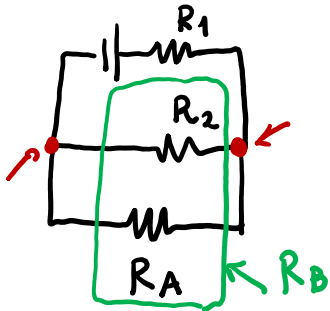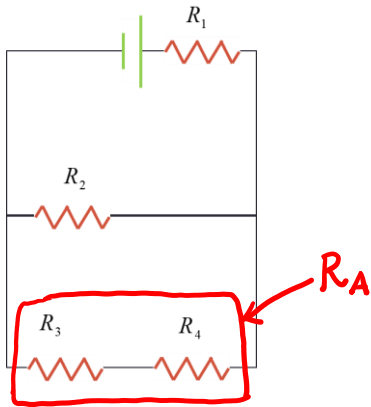


EXAMPLE 19F – WHICH LIGHTBULB WOULD BE THE BRIGHTEST IF THEY ARE ALL IDENTICAL?

$$P = I\Delta V = \underbrace{I^2 R}_{I^2 R} = \frac{\Delta V^2}{R}$$

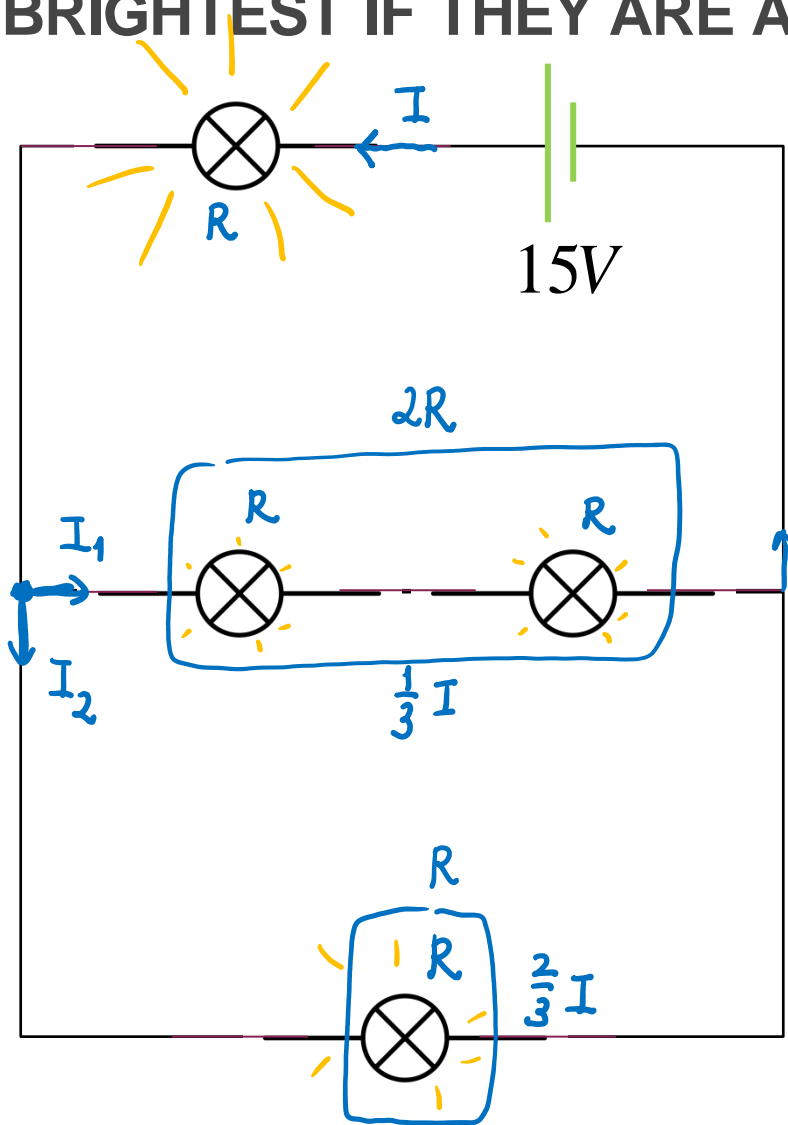


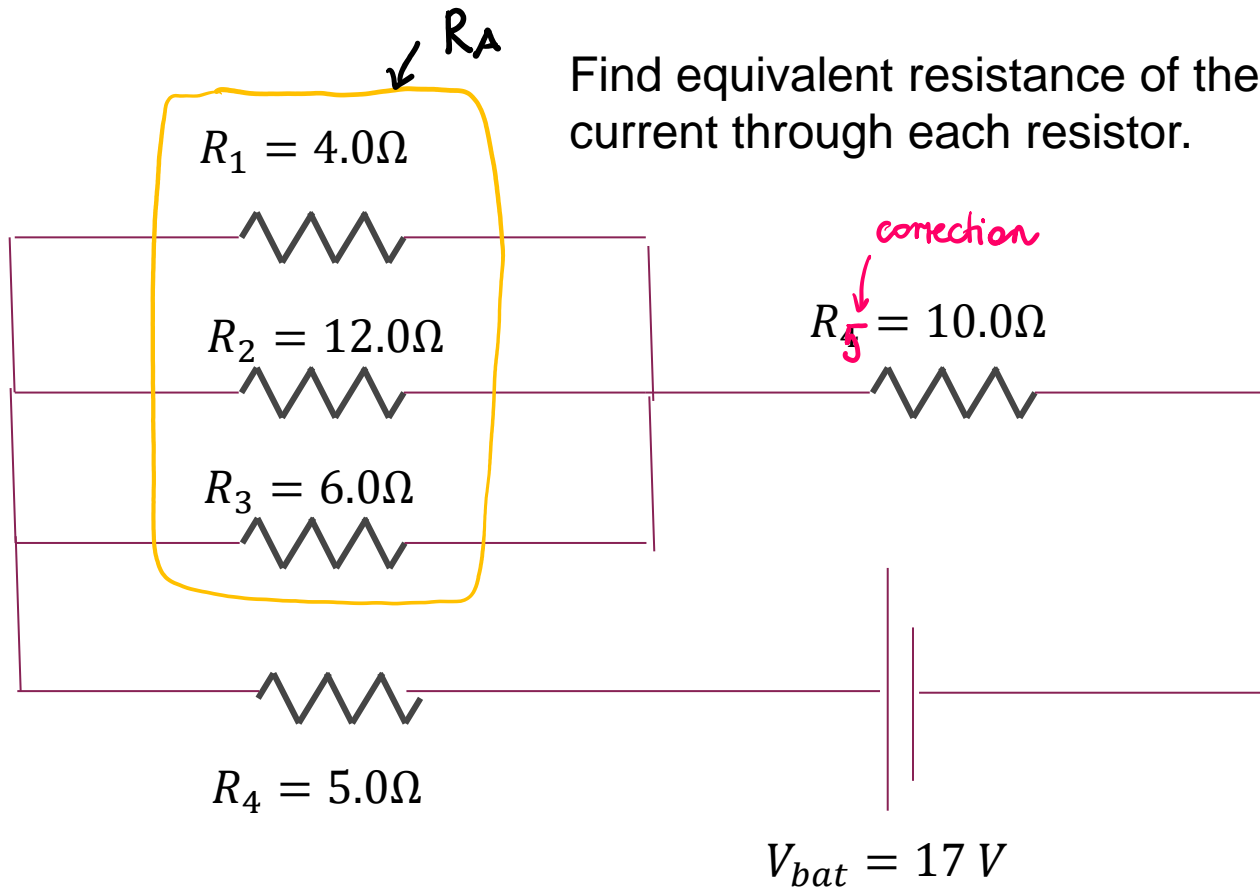
EXAMPLE 19G – A MORE COMPLICATED APPROACH



$R_A : R_1, R_2, R_3$ in parallel

$$\frac{1}{R_A} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{4} + \frac{1}{12} + \frac{1}{6} = \frac{3}{12} + \frac{1}{12} + \frac{2}{12} = \frac{6}{12}$$

$R_A = 2\Omega$

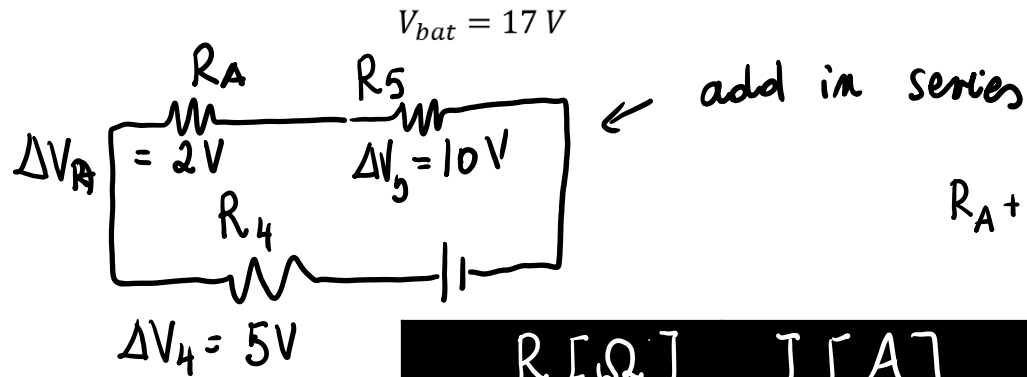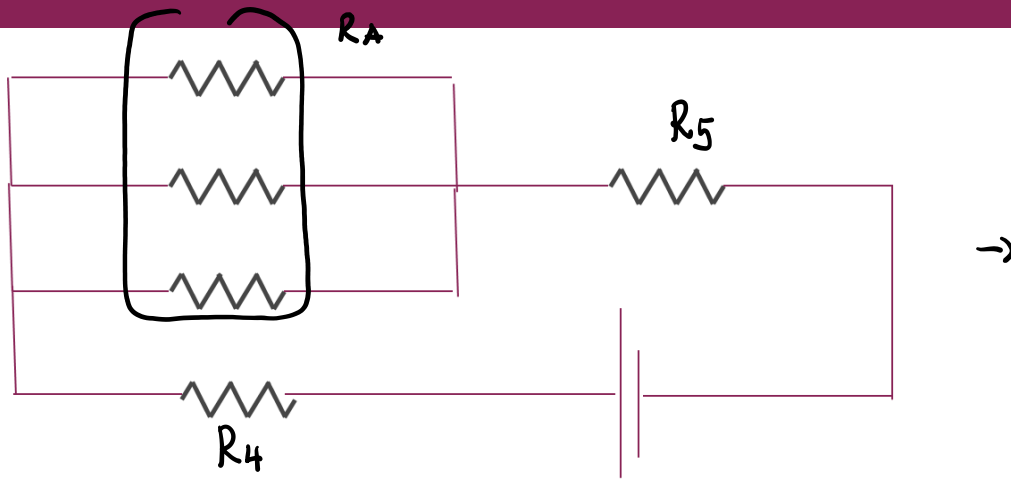

$$R_A + R_4 + R_5 = 2\Omega + 5\Omega + 10\Omega = 17\Omega$$

Table

given

$$R_A \rightarrow V_A = I_{TOT} \cdot R_A \\ = 2.0\Omega \cdot 1A = 2V$$

$R[\Omega]$	$I[A]$	$V[V]$	$P[W]$
$R_1 = 4.0$	$I = \frac{\Delta V_A}{R_1} = 0.5$	$\Delta V_A = \Delta V_1 = 2V$	1
$R_2 = 12.0$	$= \frac{1}{6}V$	$\Delta V_A = \Delta V_2 = 2V$	$\frac{1}{3}$
$R_3 = 6.0$	$= \frac{1}{3}V$	$\Delta V_A = \Delta V_3 = 2V$	$\frac{2}{3}$
$R_4 = 5.0$	all 1A	$I \cdot R_4 = 5V$	5
$R_5 = 10.0$	all 1A	$I \cdot R_5 = 10V$	10
$R_{eq} = 17\Omega$	$\epsilon_{Req} = 1$	17V	17 yay!

When analyzing circuits some people find it helpful to keep all the info in the table like this one:

Bolded values are given.


Red values are those that can be calculated once two things for a given resistor are known.

	<i>Total</i>	<i>R₁</i>	<i>R₂</i>	<i>R₃</i>	<i>R₄</i>	<i>R₅</i>
<i>R</i>	<i>R_{eq}</i>	<i>R₁</i>	<i>R₂</i>	<i>R₃</i>	<i>R₄</i>	<i>R₅</i>
<i>I</i>	$I_{total} = \frac{V_{bat}}{R_{eq}}$	<i>I₁</i>	<i>I₂</i>	<i>I₃</i>	<i>I₄</i>	<i>I₅</i>
<i>V</i>	<i>V_{bat}</i>	<i>V₁</i>	<i>V₂</i>	<i>V₃</i>	<i>V₄</i>	<i>V₅</i>
<i>P</i>	$P_{total} = V_{bat}I_{tot}$	<i>P₁</i>	<i>P₂</i>	<i>P₃</i>	<i>P₄</i>	<i>P₅</i>


As you figure out information, you just fill the table, keeping track of the information.

I don't use the tables (my brain doesn't really work that way, I prefer putting my info in the figure), but I figured I would share the technique just in case someone finds it useful.

Learning Calatytcs Problem:

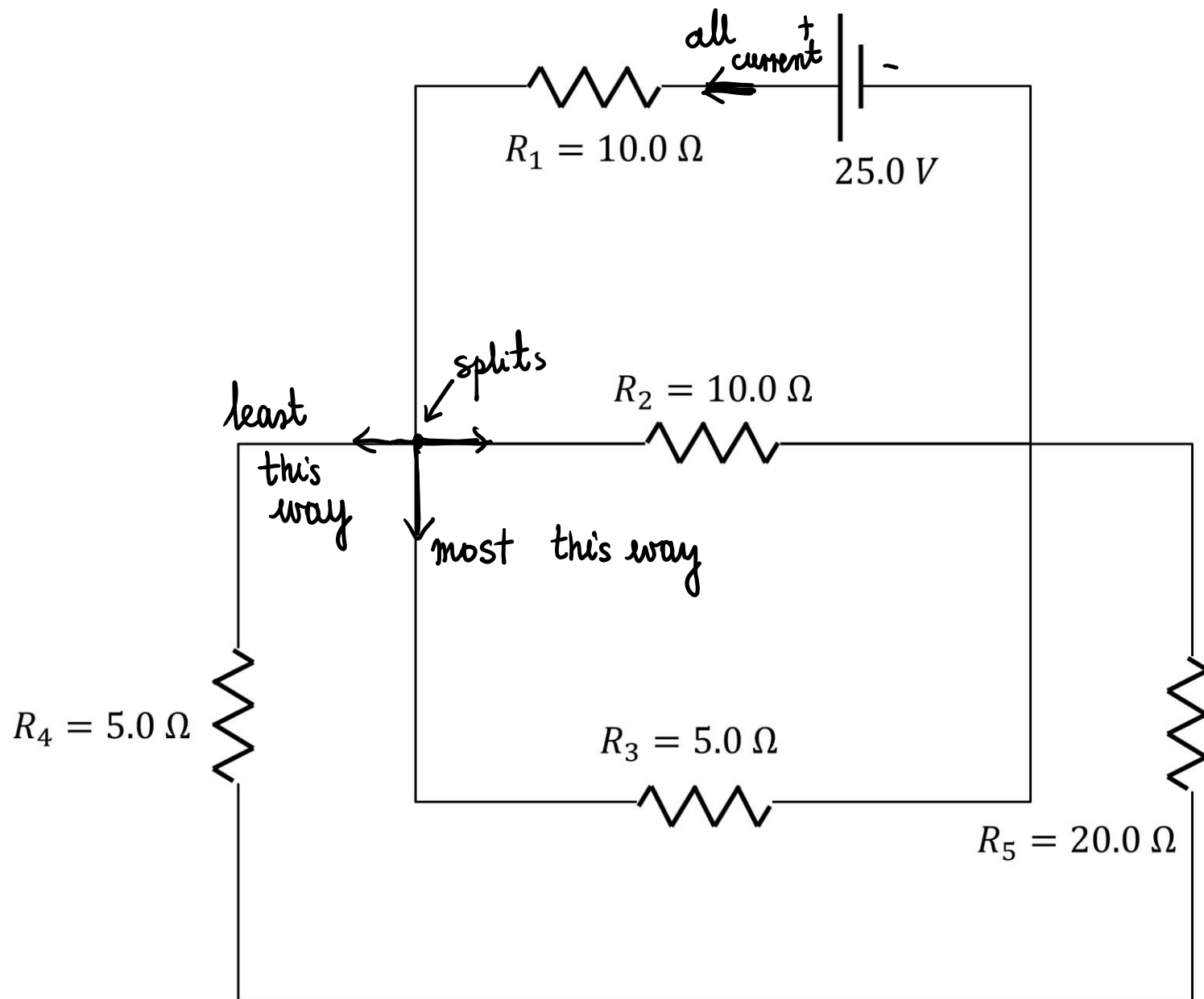


Learning Calatytics Problem:

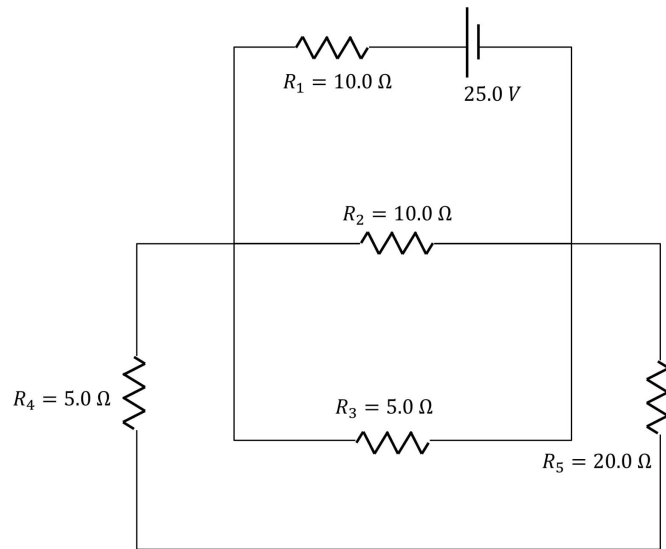


What is the equivalent resistance of R_4 and R_5 in series?

Simplified circuit:

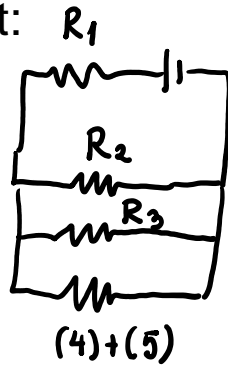


Learning Calatytics Problem:

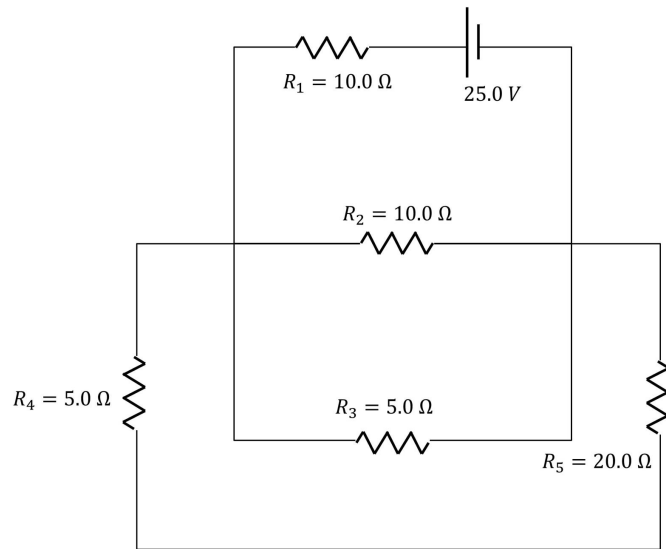

What is the equivalent resistance of R_2 and R_3 ?
in parallel!

Simplified circuit:

Learning Calatytics Problem:

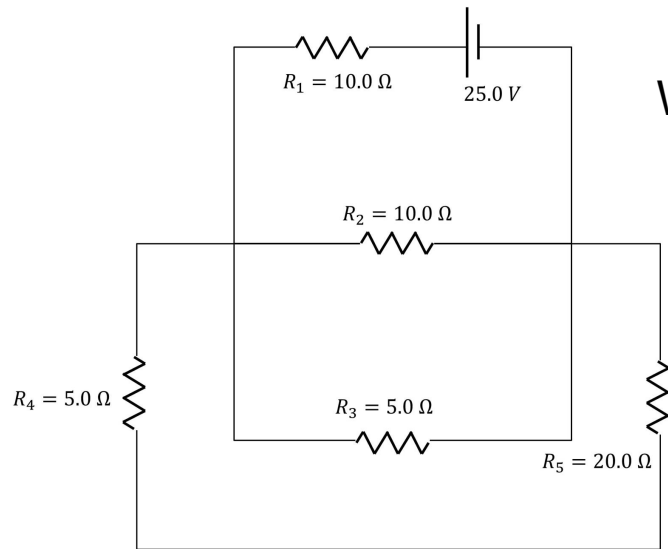


What is the equivalent resistance of R_2, R_3, R_4 and R_5 ?

R_4 & R_5 are in parallel w/ R_2 & R_3

Simplified circuit:

Learning Calatytics Problem:

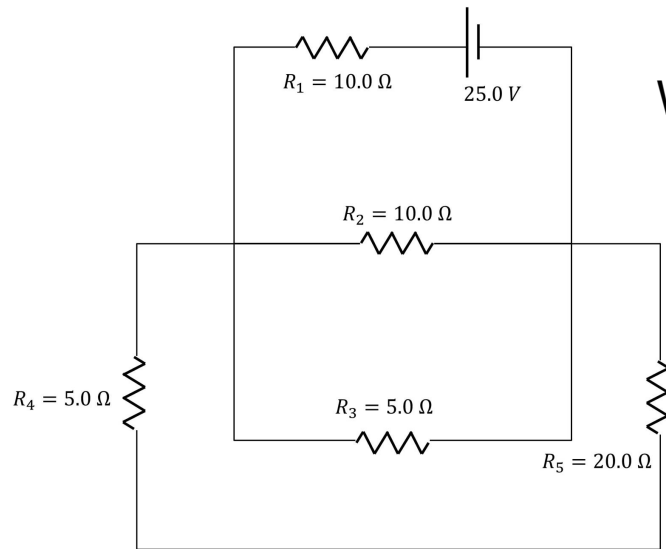

What is the equivalent resistance for this circuit?
“one resistor to replace them all”

R_1 is in series with the rest of the resistors

Simplified circuit: